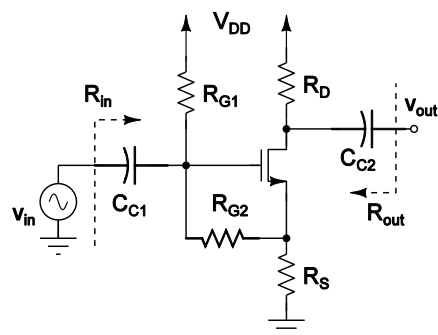


For all BJTs, assume:  $|V_{BE,on}| = 0.7V$ ,  $\beta = 100$ , and  $|V_{CE,sat}| = 0.1V$  (use  $V_T = 25mV$ ).

For all MOSFETs, assume:  $|V_{TH}| = 1V$  and  $\mu C_{ox} \frac{W}{L} = 1000 \frac{\mu A}{V^2}$ .


**Q1:** Consider the circuit shown to the right. Assume  $\frac{W}{L} = 100$ ,  $R_{G1} = 82k\Omega$ ,  $R_{G2} = 18k\Omega$ ,  $R_{S1} = 200\Omega$ ,  $R_D = 15k\Omega$ , and  $V_{DD} = 10V$ .



- What is the DC drain current,  $I_D$ , for the transistor?
- What are the minimum and maximum voltages (i.e., voltage swing) at the drain terminal of the transistor?
- Draw the small signal equivalent circuit and calculate  $g_m$ .
- What is the voltage gain,  $A_v = \frac{v_{out}}{v_{in}}$ , for the circuit?
- What are the input and output resistances of the circuit as indicated on the schematic.

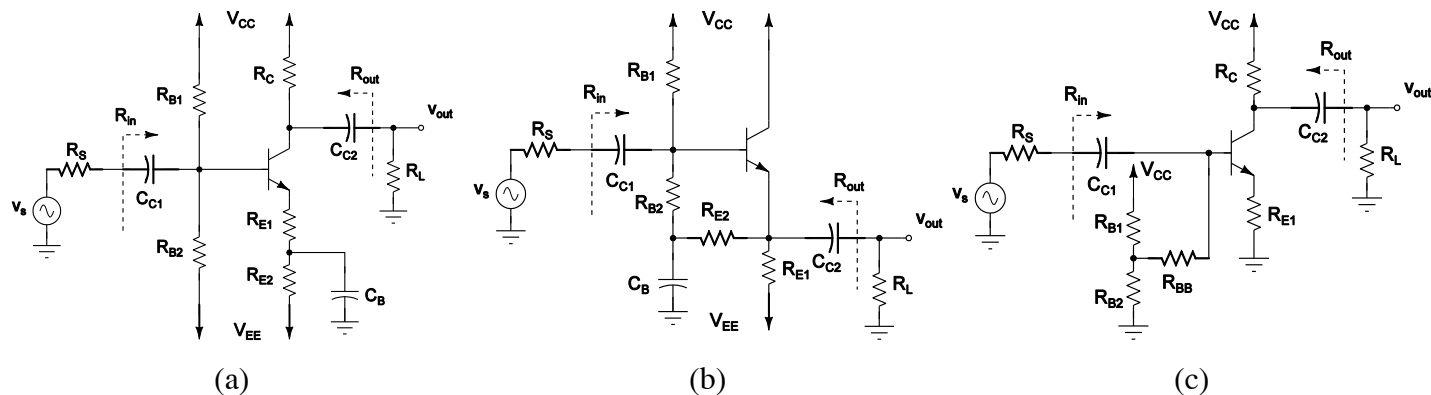**Q2:** For the circuits shown below, assume the transistors are biased with  $I_C = 1mA$  in the active region. Draw the AC (not small-signal) circuit for each case and identify each stage. Calculate the overall voltage gain,  $A_v = \frac{v_{out}}{v_s}$ , input resistance  $R_{in}$ , and output resistance  $R_{out}$  for each circuit using formulas provided inside the cover of the textbook. Write down the full expressions before inserting component values.

Resistor values are:  $R_{B1} = R_{BB} = 100k\Omega$ ,  $R_{B2} = 50k\Omega$ ,  $R_S = 10k\Omega$ ,  $R_{E1} = R_{E2} = 1k\Omega$ ,  $R_C = 5k\Omega$ , and  $R_L = 10k\Omega$ .



**Q3:** For the circuits shown below, assume the transistors are biased with  $I_D = 1mA$  in the active region. Draw the AC (not small-signal) circuit for each case and identify each stage. Calculate the overall voltage gain,  $A_v = \frac{v_{out}}{v_s}$ , input resistance  $R_{in}$ , and output resistance  $R_{out}$  for each circuit using formulas provided inside the cover of the textbook. Write down the full expressions before inserting component values.

Resistor values are:

$$R_{G1} = R_{G2} = 500k\Omega,$$

$$R_{D1} = R_{D2} = 10k\Omega,$$

$$R_{S1} = 5k\Omega,$$

$$R_L = 2k\Omega, \text{ and } R_S = 100k\Omega.$$

**Note:** The current source for circuit *a* is a DC current source.

