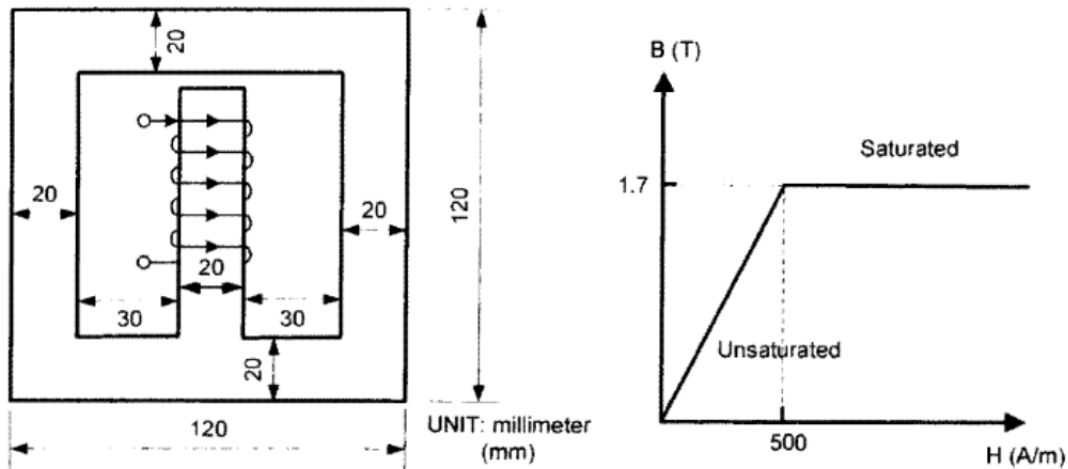


Q1. Fig. 1 shows the structure of an inductor. The unit of the dimensions is millimeter (mm). The B-H curve of the core is also shown, which is simplified from the real B-H curve with two asymptotes. The thickness of the core is 20 mm. The length of the air gap is 1 mm. The 100 turns winding is mounted on the center leg. Neglect the fringing effect and winding resistance. If the excitation voltage (voltage across the winding) is 10 V (AC rms, 60 Hz), determine the rms value of the excitation current.



Q2. Test results from a single phase, 20 kVA, 4160 V/208 V, 60 Hz transformer are as follows:

	Terminal voltage, V_t (V)	Terminal Current, I_t (A)	Input power, P_{in} (W)
Open circuit test (LV side)	208	3.2	73
Short circuit test (HV side)	153	2.6	54

- Determine the parameters (R_{eq} , X_{eq} , R_c , and X_m) of the transformer referred to the HV side.
- Draw the approximate equivalent circuit of the transformer referred to the HV side.

Q3. A shunt dc motor has the rated armature current of 40 A. The total resistance in the armature circuit is 0.3 Ω and the total resistance in the field circuit is 100 Ω . When the shunt motor is connected to a 180 V power supply, the terminal current is 4.8 A and the motor rotates at 1500 rpm without any mechanical load. Assuming that the terminal voltage remains at 180V and the rotational loss is constant, answer the following questions:


- Calculate rotational loss P_{rot} ,
- Calculate speed and torque at the rated armature current, assuming no armature reaction,
- Calculate the efficiency at the rated armature current, assuming no armature reaction,

- d) Calculate the speed, torque at the rated armature current assuming a 6% flux reduction due to armature reaction.

Q4. A **440 V, 60 Hz**, Y-connected, 4-pole slip ring (wound rotor) induction motor has the following circuit parameters: $R_1 = 0.6\Omega$, $R_2' = 0.5\Omega$, $X_1 = X_2' = 0.8\Omega$, $X_m = 50\Omega$, calculate the following:

- a) The starting line current (stator current) I_1 ,
- b) Starting torque T_{st} ,
- c) Speed of rotation n in rpm when the shaft developed torque is **160 Nm**
- d) Maximum developed torque, T_{max}

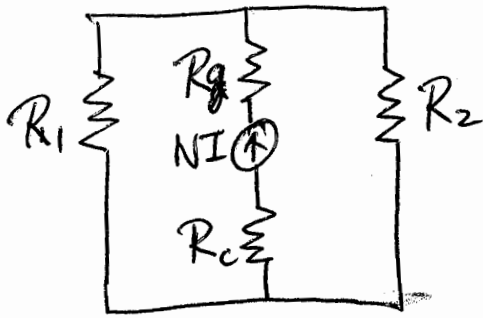Q1. If $B_c = 1.7 \text{ T}$, $\mu_c = 1.7/500 = 0.0034$ $A = 20 \times 20 = 400 \text{ mm}^2$



$$R_g = \frac{l_g}{\mu_0 A} = \frac{1 \times 10^{-3}}{4\pi \times 10^7 \times (0.02 \times 0.02)}$$

$$= 1.9894 \times 10^6$$

$$R_c = \frac{l_c}{\mu_c A} = 7.3529 \times 10^4$$

$$R_1 = R_2 = 1.4705 \times 10^5$$

$V = E = 10 \text{ V} = 4.44 f N \phi_{pk} \rightarrow \phi_{pk} = \frac{10}{4.44 \times 60 \times 100}$
 (no resistance) $= 3.7538 \times 10^{-4} \text{ Wb}$

$$B_{pk} = \frac{\phi_{pk}}{A} = 0.9384 \text{ T} < 1.7 \text{ T}$$

$$NI_{pk} = \phi_{pk} \cdot R_t \Rightarrow I = \frac{\phi_{pk} \cdot R_t}{N \cdot \sqrt{2}} = \frac{3.7538 \times (R_1 // R_2 + R_c + R_g)}{100 \times \sqrt{2}}$$

$$= 5.6709 \text{ A}$$

$$Q2 \ a) \ R_{eq} = 7.988 \Omega \quad X_{eq} = 58.3 \Omega \quad R_c = 237.06 \text{ k}\Omega \quad X_m = 26.16 \text{ k}\Omega$$

$$R_{c,LV} = \frac{V_t^2}{P} = \frac{208^2}{73} = 592.66 \Omega$$

$$I_c = V_t / R_{c,LV} = 208 / 592.66 = 0.35096 \text{ A}$$

$$I_m = \sqrt{I_t^2 - I_c^2} = \sqrt{3.2^2 - 0.35096^2} = \sqrt{10.1168} = 3.1807 \text{ A}$$

$$X_{m,LV} = V_t / I_m = 208 / 3.1807 = 65.39 \Omega$$

referred to the HV side :


$$R_c = a^2 R_{c,LV} = \left(\frac{4160}{208}\right)^2 592.66 = 237.064 \text{ k}\Omega$$

$$X_m = a^2 X_{m,LV} = 20^2 \times 65.39 = 26.16 \text{ k}\Omega$$

$$R_{eq} = P / I_t^2 = 54 / 2.6^2 = 7.9882 \Omega$$

$$X_{eq} = \sqrt{(V_t / I_t)^2 - (R_{eq})^2} = \sqrt{\left(\frac{153}{2.6}\right)^2 - 7.9882^2} = \sqrt{3399.06} = 58.3 \Omega$$

b)

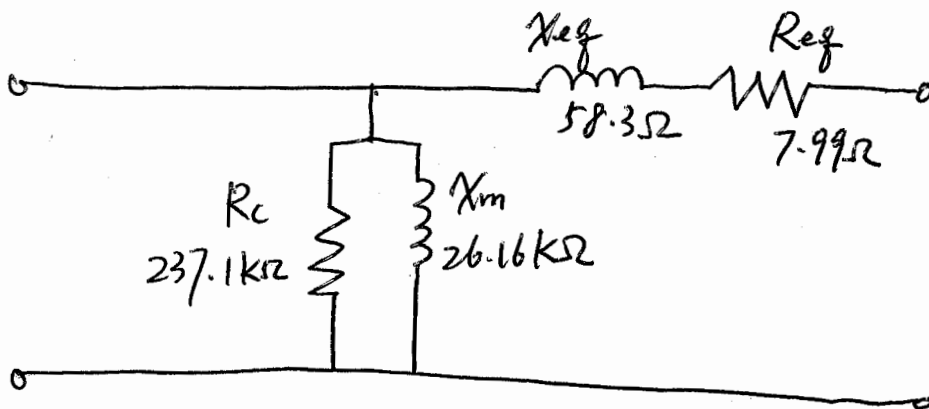

Q3. a) $P_{rot} = 537.3 \text{ W}$

$$I_f = V_t / R_f = 180 / 100 = 1.8 \text{ A}, I_a = I_t - I_f = 4.8 - 1.8 = 3 \text{ A}$$

$$P_{ele} = E_{a,NL} I_{a,NL} = (V_t - I_a R_a) I_a = (180 - 0.3 \times 3) \times 3 = 537.3 \text{ W}$$

$$P_{rot} = P_{ele} = 537.3 \text{ W}$$

b) $n = 1407.26 \text{ rpm} \quad T = 45.6 \text{ Nm}$

$$E_{a,NL} = V_t - I_a R_a = 180 - 0.3 \times 3 = 179.1 \text{ V}$$

$$\omega_{NL} = \frac{1500}{60} \times 2\pi = 157.08 \text{ rad/s}$$

$$K_a \phi = E_{a,NL} / \omega_{NL} = 179.1 / 157.08 = 1.14 \text{ V} \cdot \text{sec/rad}$$

$$E_{a,FL} = V_t - I_a R_a = 180 - 0.3 \times 40 = 168 \text{ V}$$

$$\omega_{FL} = E_{a,FL} / K_a \phi = 168 / 1.14 = 147.368 \text{ rad/s}$$

$$n = \frac{\omega_{FL}}{2\pi} \times 60 = \frac{147.386}{2\pi} \times 60 = 1407.26 \text{ rpm}$$

$$T = K_a \phi I_a = 1.14 \times 40 = 45.6 \text{ Nm}$$

c) $\eta = 0.822$

$$P_m = V_t (I_f + I_a) = 180 \times (40 + \frac{180}{100}) = 7524 \text{ W}$$

$$P_{ele} = E_{a,FL} I_{a,FL} = 168 \times 40 = 6720 \text{ W}$$

$$P_{out} = P_{ele} - P_{rot} = 6720 - 537.3 = 6182.7 \text{ W}$$

$$\eta = P_{out} / P_m = 6182.7 / 7524 = 0.822$$

$$d) \quad n = 1497.1 \text{ rpm} \quad T = 42.864 \text{ Nm}$$

$$K_a \phi_{FL} = 0.94 K_a \phi_{NL} = 0.94 \times 1.14 = 1.0716 \text{ V} \cdot \text{sec/rad}$$


$$E_{a,FL} = V_t - I_a R_a = 180 - 0.3 \times 40 = 168 \text{ V}$$

$$\omega_{FL} = \frac{E_{a,FL}}{K_a \phi_{FL}} = \frac{168}{1.0716} = 156.775 \text{ rad/s}$$


$$n = \frac{\omega_{FL}}{2\pi} \times 60 = \frac{156.775}{2\pi} \times 60 = 1497.1 \text{ rpm}$$

$$T = K_a \phi_{FL} I_a = 1.0716 \times 40 = 42.864 \text{ Nm}$$

Q4. IEEE equivalent circuit of the motor

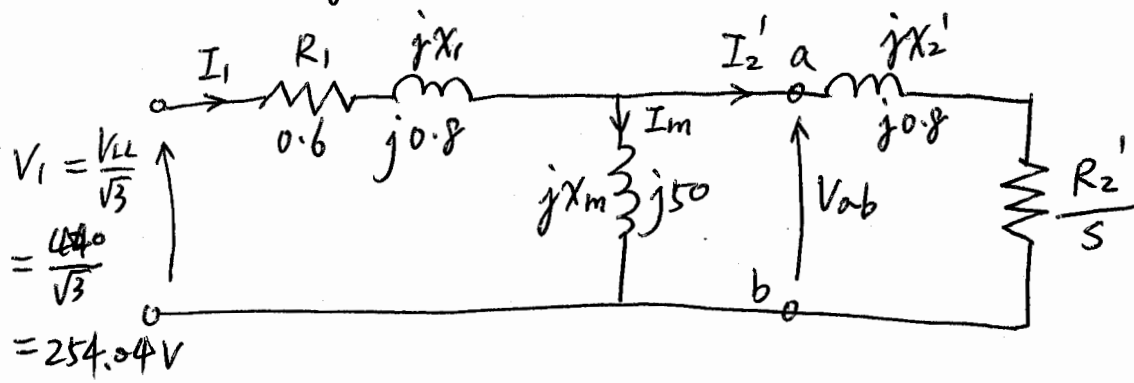

Thevenize the circuit at a-b

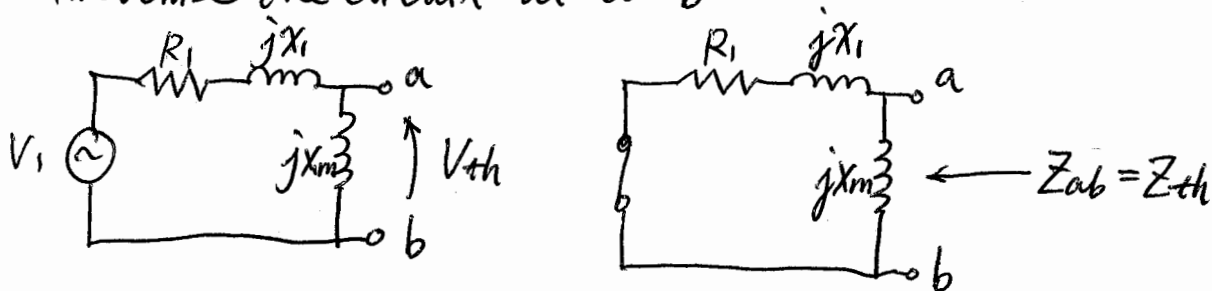


$$V_{th} = V_{ab} = \frac{jX_m}{R_1 + j(X_1 + X_m)} V_1 = \frac{j50}{0.6 + j50.8} \cdot V_1 = 0.984 \angle 0.7^\circ \cdot V_1$$

$$V_1 = 254.04V \Rightarrow V_{th} = 0.984 \angle 0.7^\circ (254.04 \angle 0^\circ) = 249.98 \angle 0.7^\circ$$

$$Z_{th} = (R_1 + jX_1) // jX_m = \frac{jX_m(R_1 + jX_1)}{R_1 + j(X_1 + X_m)} = \frac{j50(0.6 + j0.8)}{0.6 + j50.8}$$

$$= 0.984 \angle 53.83^\circ$$

$$= 0.581 + j0.794 \Omega$$

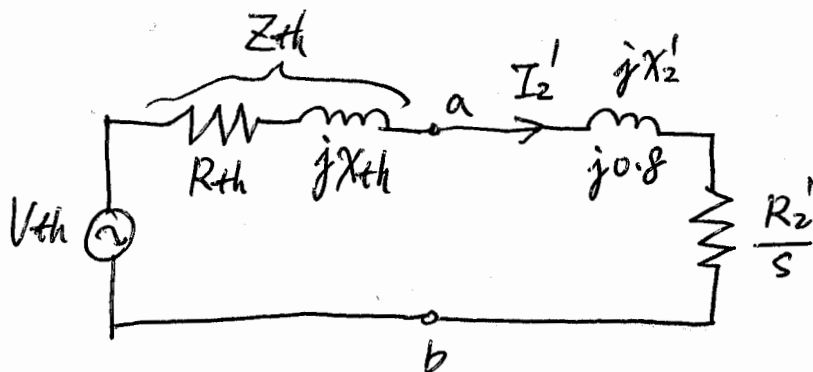

a) Z_T at any speed or slip is $Z_T = Z_{th} + jX_2' + \frac{R_2'}{s} = 0.581 + j0.794 + j0.8 + \frac{0.5}{s}$

When starting, $n_r = 0 \Rightarrow s = \frac{n_s - n_r}{n_s} = \frac{n_s - 0}{n_s} = 1$

$\therefore Z_T = 0.581 + j0.794 + j0.8 + \frac{0.5}{1} = 1.081 + j1.594 = 1.926 \angle 55.86^\circ (\Omega)$

$I_2' = \frac{V_{th}}{Z_T} = \frac{249.98 \angle 0.7^\circ}{1.926 \angle 55.86^\circ} = 129.792 \angle -55.16^\circ (A)$

$\therefore V_{ab} = I_2' \left(\frac{R_2'}{1} + jX_2' \right) = 129.792 \angle -55.16^\circ (0.5 + j0.8)$
 $= 129.792 \angle -55.16^\circ (0.9434 \angle 57.995^\circ)$
 $= 122.45 \angle 2.84^\circ (V)$

now go back to ~~IEEE~~ equivalent circuit to calculate I_m and I_1

$I_m = V_{ab} / jX_m = \frac{122.45 \angle 2.84^\circ}{50 \angle 90^\circ} = 2.449 \angle -87.16^\circ (A)$

$I_1 = I_2' + I_m = 129.792 \angle -55.16^\circ + 2.449 \angle -87.16^\circ$
 $= 131.881 \angle -55.73^\circ (A)$

b) $T = 3 \frac{(I_2')^2 \frac{R_2'}{s}}{\omega_s}$, at starting, $s = 1$

$n_s = \frac{120f}{p} = \frac{120(60)}{4} = 1800 \text{ rpm}$ $\omega_s = \frac{1800}{60} \cdot 2\pi = 188.5 \text{ rad/sec}$

$T_{st} = 3 \cdot \frac{(129.792)^2 \left(\frac{0.5}{1} \right)}{188.5} = 134.053 \text{ Nm}$

c) Torque at any slip $T = \frac{3}{\omega_s} (I_2')^2 \frac{R_2'}{s}$

From the thevenin equivalent circuit

$$|I_2'| = \frac{|V_{th}|}{\sqrt{(R_{th} + \frac{R_2'}{s})^2 + (X_{th} + X_2')^2}} \Rightarrow |I_2'|^2 = \frac{(249.98)^2}{(0.581 + \frac{0.5}{s})^2 + (1.594)^2}$$

$$T = 160 = \frac{3}{188.5} \cdot \frac{(249.98)^2}{(0.581 + \frac{0.5}{s})^2 + (1.594)^2} \cdot (\frac{0.5}{s})$$

$$160 = \frac{497.268 \cdot s}{2.879s^2 + 0.531s + 0.25} \Rightarrow 2.879s^2 - 2.577s + 0.25 = 0$$

$$\Rightarrow S_1 = 0.111 \text{ \& } S_2 = 0.785$$



S_2 operates in unstable region, only S_1 is acceptable

$$\begin{aligned} \therefore n &= (1 - S_1)n_s \\ &= (1 - 0.111)1800 = 1600.2 \text{ rpm} \end{aligned}$$

d) at T_{max} , $\frac{R_2'}{S_m} = \sqrt{R_{th}^2 + (X_{th} + X_2')^2}$

$$\Rightarrow S_m = \frac{R_2'}{\sqrt{R_{th}^2 + (X_{th} + X_2')^2}}$$

$$= \frac{0.5}{\sqrt{(0.581)^2 + (0.794 + 0.8)^2}} = 0.295$$

Calculate I_2' using Thevenin circuit

$$I_2' = \frac{V_1}{(R_{th} + \frac{R_2'}{S_m}) + j(X_{th} + X_2')} = \frac{249.98 \angle 0.7^\circ}{(0.581 + \frac{0.5}{0.295}) + j(0.794 + 0.8)}$$
$$= 89.953 \angle 34.31^\circ (\text{A})$$

$$\therefore T_{max} = \frac{3}{\omega_s} (I_2')^2 \frac{R_2'}{S_m} = \frac{3}{188.5} (89.953)^2 \left(\frac{0.5}{0.295}\right) = 218.27 \text{ N}\cdot\text{m}$$