

Q1

A one-quadrant chopper is used to charge the battery as shown in Fig.1. The input dc voltage of the chopper is **150V**. The output of the chopper is connected to the battery through a **2.5mH** inductor. As shown in Fig.2, two charging stages are implemented by the controller, which adjusts the duty cycle of the chopper: 1) when the battery's voltage is lower than 24V, a **20A** constant charging current is applied to the battery; 2) when the battery's voltage is higher than 24V, a **1A** constant charging current is applied to charge the battery to full. The switching frequency of the chopper is **1000Hz**. Assume the internal impedance of the battery is zero and the battery's voltage is constant during each switching cycle.

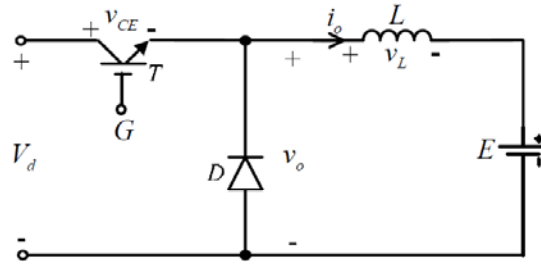


Figure 1 Battery charger

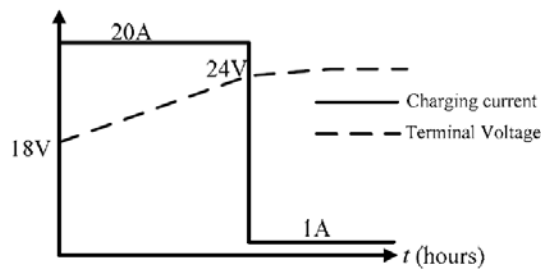


Figure 2 Two stages charging

At the beginning, the battery's voltage is **18V** and the average charge current is **20A**. Answer questions 1) and 2).

1) Determine the operation mode of the chopper.

Solution:

$$\text{Assume it's in continuous current mode} \rightarrow V_o = DV_d \rightarrow D = V_o/V_d = 18/150 = 0.12$$

$$\therefore I_{LB} = \frac{T_s V_d}{2L} D(1-D) = \frac{1 \times 10^{-3} \times 150}{2 \times 2.5 \times 10^{-3}} \times 0.12 \times (1-0.12) = 3.168 \text{ A}$$

$$\therefore I_L = I_o = 20\text{A} > I_{LB}$$

\therefore The charger is running in continuous current mode

2) Find the duty cycle, D .

Solution:

\therefore It's running in continuous current mode

$$\therefore V_o = DV_d \rightarrow$$

$$D = V_o/V_d = 18/150 = 0.12$$

After few hours of charging, the battery's voltage reaches **24V** and a **1A** average current is applied to the battery. Answer questions 3) ~ 5)

3) Determine the operation mode of the chopper.

Solution:

Assume it's in continuous current mode $\rightarrow V_o = DV_d \rightarrow D = V_o/V_d = 24/150 = 0.16$

$$\therefore I_{LB} = \frac{T_s V_d}{2L} D(1-D) = \frac{1 \times 10^{-3} \times 150}{2 \times 2.5 \times 10^{-3}} \times 0.16 \times (1-0.16) = 4.032 \text{ A}$$

$$\therefore I_L = I_o = 1\text{A} < I_{LB}$$

\therefore The charger is running in discontinuous current mode

4) Find the duty cycle, D .

Solution:

It's running in discontinuous current mode

$$V_o = \frac{D^2}{D^2 + \frac{1}{4}(I_o/I_{LB,\max})} V_d, \text{ where } I_{LB,\max} = \frac{T_s V_d}{8L} = \frac{1 \times 10^{-3} \times 150}{8 \times 2.5 \times 10^{-3}} = 7.5 \text{ A}$$


$$D = \sqrt{\frac{\frac{V_o}{4}(I_o/I_{LB,\max})}{V_d - V_o}} = \sqrt{\frac{\frac{24}{4}(1/7.5)}{150 - 24}} = 0.0797$$

5) Sketch to scale the following waveforms, indicating the peak values.

i) voltage waveform of the inductor, v_L .

ii) output current waveform, i_o

iii) output voltage waveform, v_o

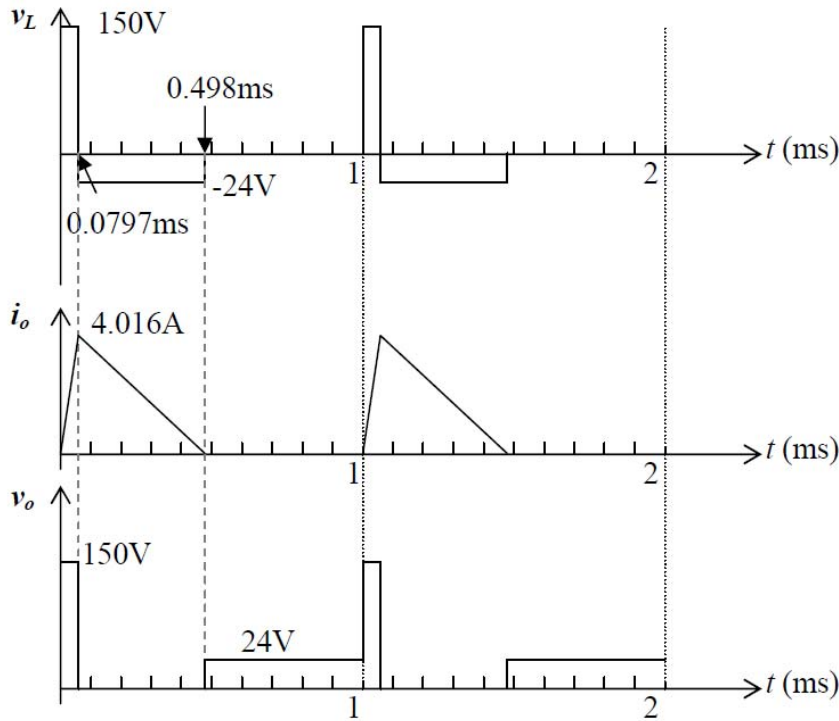

$$\Delta_1 = \frac{I_o}{4I_{LB,\max}D} = \frac{1}{4 \times 7.5 \times 0.0797} = 0.4183$$

$$I_{L,\max} = \frac{V_d - V_o}{L} t_{on} = \frac{150 - 24}{2.5 \times 10^{-3}} \times 0.0797 \times 10^{-3} = 4.016 \text{ A}$$

Q2

a) The converter is running in continuous current mode.

$$D = V_o/V_d = 5/15 = 0.333$$

$$b) \Delta I = \frac{V_d - V_o}{L} \cdot t_{on} = \frac{V_o}{L} \cdot t_{off}$$

$$\text{Method 1: } L = \frac{V_d - V_o}{\Delta I_L} \cdot \frac{D}{f_s} = 0.1667 \text{ mH}$$

$$\text{Method 2: } L = \frac{V_o}{\Delta I_L} \cdot \frac{(1-D)}{f_s} = 0.1667 \text{ mH}$$

$$c) \Delta V_o = \frac{\Delta I_L}{8} \cdot \frac{1}{f_s C} \rightarrow C = \frac{\Delta I_L}{8 \Delta V_o \cdot f_s} = \frac{1}{8 \times 10 \times 10^{-2} \times 20 \times 10^3}$$
$$= 625 \text{ nF}$$

$$d) I_{LB} = \frac{1}{2} i_{L, \text{peak}} = \frac{1}{2} \times 1 = 0.5 \text{ A}$$

$$I_{OB} = I_{LB} = 0.5 \text{ A}$$

Q3


$$a) V_o = 5V, R_L = 20\Omega \rightarrow I_o = \frac{V_o}{R_L} = 0.25A$$

$I_o < I_{oB} \rightarrow$ The converter is running in DCM.

$$I_{LB, \max} = \frac{T_s V_d}{8L} = \frac{V_d}{8f_s L} = \frac{15}{8 \times 20 \times 10^3 \times 0.1667 \times 10^{-3}} = 0.5625A$$

$$D = \sqrt{\frac{V_o (I_o / I_{LB, \max})}{V_d - V_o}} = \sqrt{\frac{5 \times (0.25 / 0.5625)}{15 - 5}} = 0.2357$$
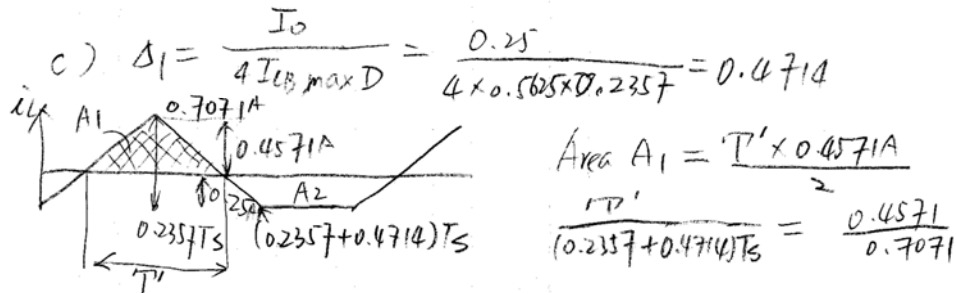
$$b) \Delta I_L = \frac{V_d - V_o}{L} \cdot t_{on} = \frac{15 - 5}{0.1667 \times 10^{-3}} \times \frac{0.2357}{20 \times 10^3} = 0.7071A$$



$$T' = \frac{0.4571}{0.7071} \cdot (0.2357 + 0.4714)T_s = 22.85\mu s$$




$$\Delta V_C = \frac{\text{Area } A_1}{C} = \frac{22.85 \times 0.4571}{2C} = 8.4mV$$

$$\Delta V_o = \Delta V_C = 8.4mV$$

$$\text{or } \Delta V_C = \frac{\text{Area } A_2}{C} = \frac{(T_s - T') + (1 - D - \Delta I)T_s}{2C} \times I_o = \frac{(50 - 22.85) + (1 - 0.2357 - 0.4714) \times 50}{2 \times 625} \times 0.25$$

$$= 8.4mV$$

Q4

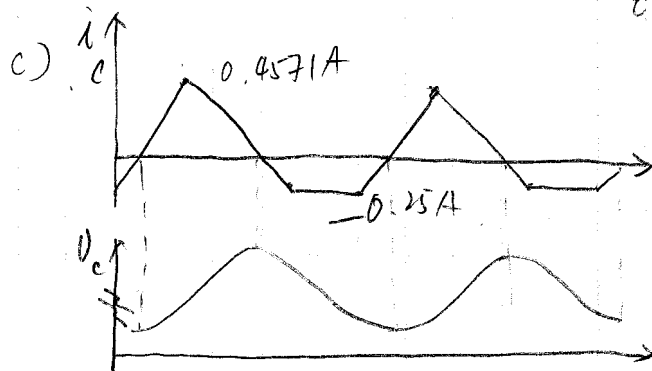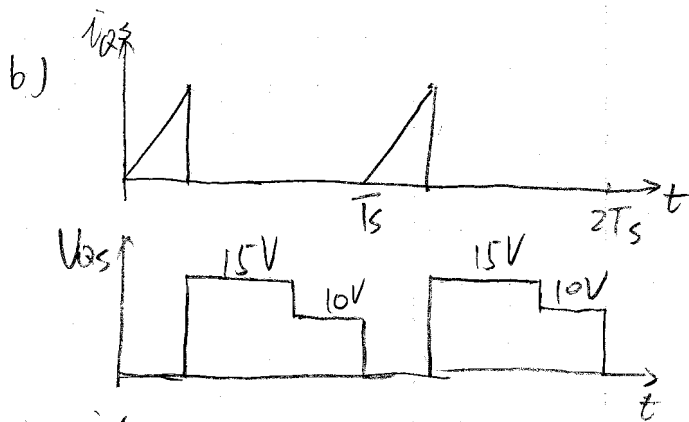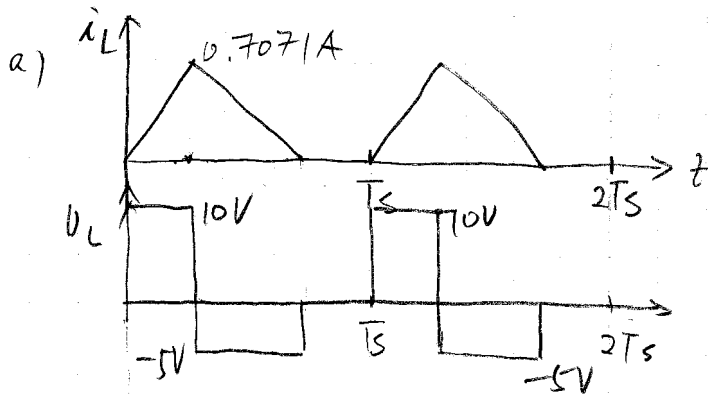

Q5

a) Assume CCM $t_{on} = D/f_s = 0.8 \text{ ms}$ $\tau = L/R = 1.5 \text{ ms}$ $T_s = \frac{1}{f_s} = 2 \text{ ms}$

$$I_{min} = \frac{V_d}{R} \frac{e^{t_{on}/\tau} - 1}{e^{T_s/\tau} - 1} = \frac{E}{R} = -85.84 \text{ A} < 0 \quad \therefore \text{DCM, } I_{min} = 0$$

b) $t_x = \tau \ln \left\{ e^{t_{on}/\tau} \left[1 + \frac{V_d - E}{E} (1 - e^{-t_{on}/\tau}) \right] \right\} = 0.0016 \text{ s} = 1.6 \text{ ms}$

$$V_{a,avg} = \frac{t_{on}}{T_s} V_d + \frac{T_s - t_x}{T_s} E = 141.55 \text{ V}$$

$$I_{a,avg} = \frac{V_{a,avg} - E}{R} = \frac{141.55 - 110}{0.4} = 78.87 \text{ A}$$

c) $I_{a,max} = \frac{V_d - E}{R} (1 - R^{-t_{on}/\tau}) = 196.34 \text{ A}$

