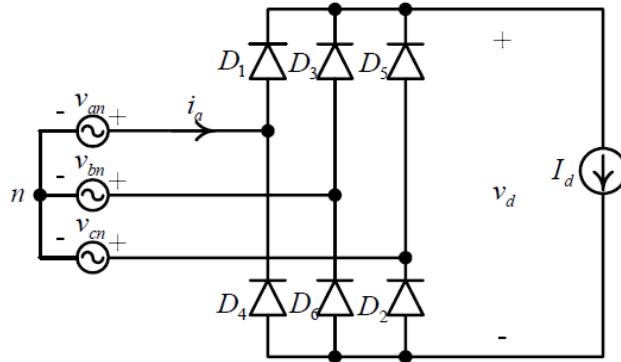



### Question 1

Consider the three-phase full-bridge diode rectifier shown below. Assuming the input line-to-line voltage  $V_{LL} = 208 \text{ V}$  (60 Hz), and dc current  $I_d = 20 \text{ A}$ . All the diodes are ideal. Answer the following questions.



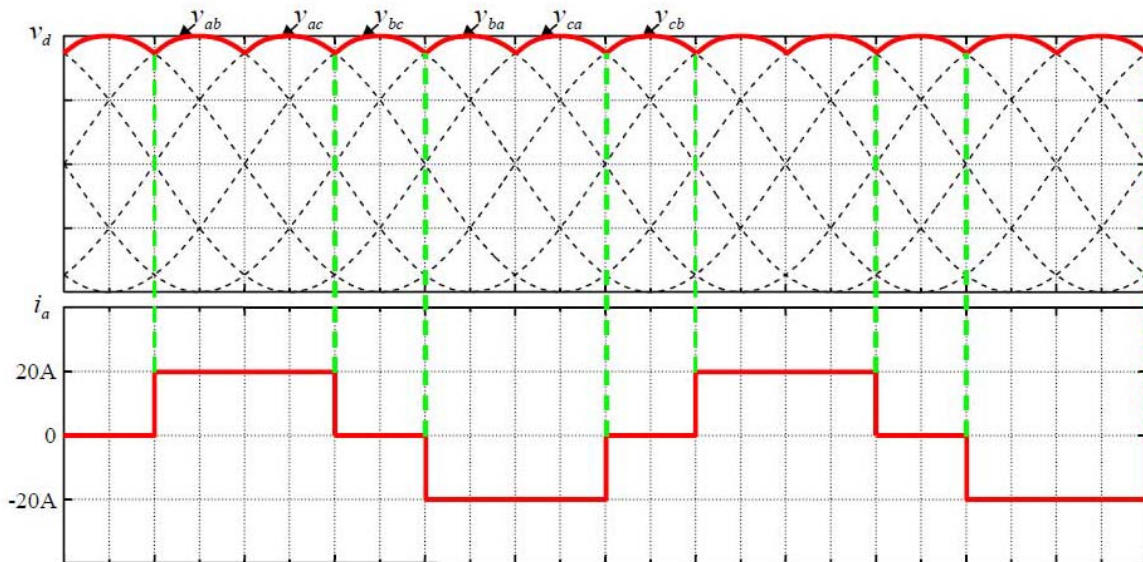- 1) Using the waveform template below, draw the following waveforms.

Voltage waveform  $v_d$ , and line current waveform  $i_a$



- 2) Calculate the **average** value of  $v_d$

$$V_{d,avg} = 280.9 \text{ V}$$

Solution:

$$V_{d,avg} = \frac{3\sqrt{2}}{\pi} V_{LL} = 1.35V_{LL} = 1.35 \times 208 = 280.9 \text{ V}$$

- 3) Calculate the **rms** value of  $v_d$

$$V_{d,rms} = 281.15 \text{ V}$$

Solution:

$$\begin{aligned} V_{d,rms} &= \sqrt{\frac{1}{\pi/3} \int_{\pi/3}^{2\pi/3} (\sqrt{2}V_{LL} \sin \omega t)^2 d\omega t} \\ &= \sqrt{\frac{V_{LL}^2}{\pi/3} \int_{\pi/3}^{2\pi/3} 2 \sin^2 \omega t d\omega t} = \sqrt{\frac{V_{LL}^2}{\pi/3} \int_{\pi/3}^{2\pi/3} (1 - \cos 2\omega t) d\omega t} \\ &= \sqrt{\frac{V_{LL}^2}{\pi/3} \left( \omega t - \frac{\sin 2\omega t}{2} \right) \Big|_{\pi/3}^{2\pi/3}} = V_{LL} \sqrt{1 + \frac{3\sqrt{3}}{2\pi}} \\ &= 1.3517V_{LL} = 1.3517 \times 208 = 281.15 \text{ V} \end{aligned}$$

4) Calculate the **rms** value of line current  $i_d$

$$I_{a,rms} = 16.33 \text{ A}$$

Solution:

$$I_{a,rms} = \sqrt{\frac{2}{3}} I_d = 0.816 I_d = 0.816 \times 20 = 16.33 \text{ A}$$

5) Calculate the **total** input power of the converter,  $P_{in}$

$$P_{in} = 5.62 \text{ kW}$$

Solution:


$$PF = \frac{3}{\pi} = 0.955$$

$$P_{in} = \sqrt{3} V_{LL} I_{a,rms} PF = \sqrt{3} \times 208 \times 16.33 \times 0.955 = 5.62 \text{ kW}$$

$$\text{or } P_{in} = P_{out} = V_{d,avg} I_d = 280.9 \times 20 = 5.62 \text{ kW}$$
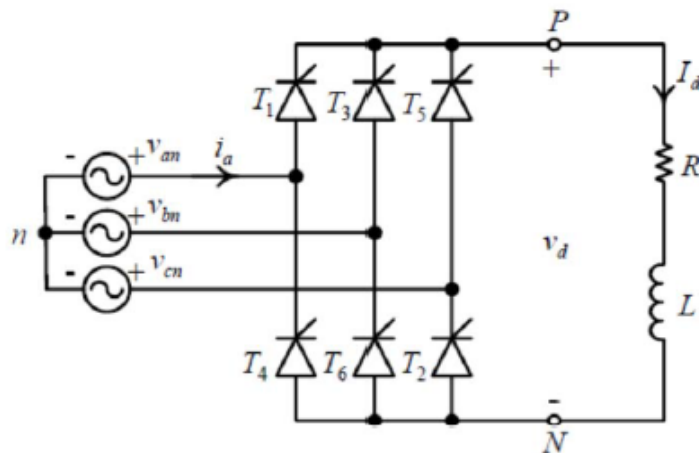
## Question 2

A three-phase full bridge SCR rectifier with RL load is shown below. The load resistance is  $20 \Omega$  and inductance is very large. The input **line-to-line** voltage of the rectifier is 480 V (60 Hz). The firing angle for the SCR devices is 60 degree. Answer the following questions.



- 1) Find the load current  $I_d$

$$I_d = \underline{16.2} \text{ A}$$

Solution:

$$V_d = 1.35V_{LL} \cos \alpha = 1.35 \times 480 \times \cos 60^\circ = 324 \text{ V}$$

$$I_d = \frac{V_d}{R} = \frac{324}{20} = 16.2 \text{ A}$$

- 2) Calculate the total power factor at the line side (input side),  $PF =$  \_\_\_\_\_

$$PF = \underline{0.4475}$$

Solution:

$$PF = 0.955 \cos \alpha = 0.955 \times \cos 60^\circ = 0.4775$$

- 3) Calculate the total input power  $P_{input}$

$$P_{input} = \underline{5.25} \text{ kW}$$

Solution:


$$I_L = \sqrt{\frac{2}{3}} I_d = \sqrt{\frac{2}{3}} \times 16.2 = 13.2272 \text{ A}$$

$$P_{input} = \sqrt{3} V_{LL} I_L \times PF = \sqrt{3} \times 480 \times 13.2272 \times 0.4775 = 5.25 \text{ kW}$$

or


$$P_{input} = P_{out} = V_d I_d = 324 \times 16.2 = 5.25 \text{ kW}$$

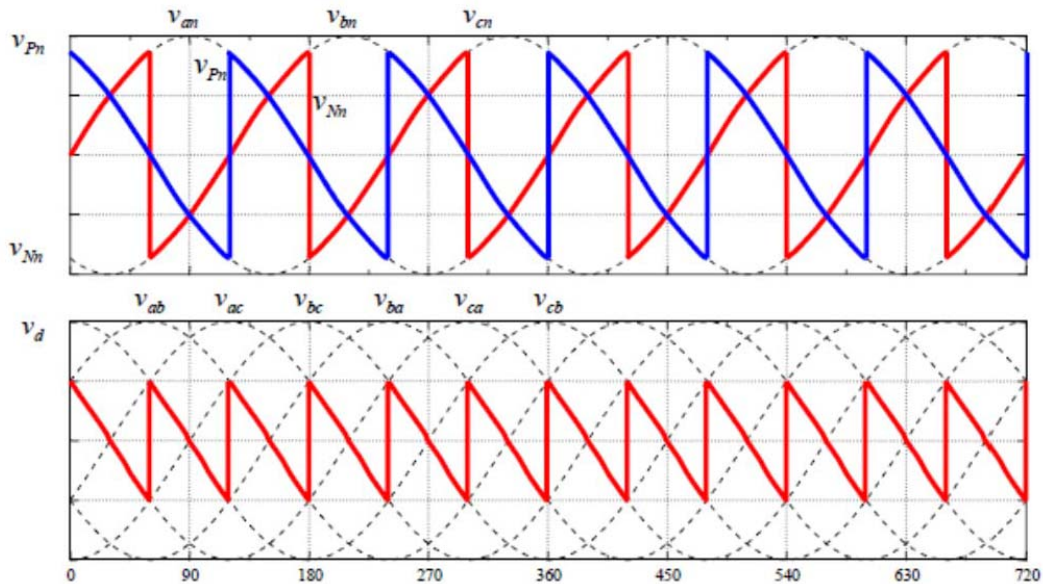- 4) Using the waveform template below draw the voltage waveforms of  $v_{Pn}$ ,  $v_{Nn}$  and  $v_d$ , assuming the firing angle is 90 degrees and load current is constant.


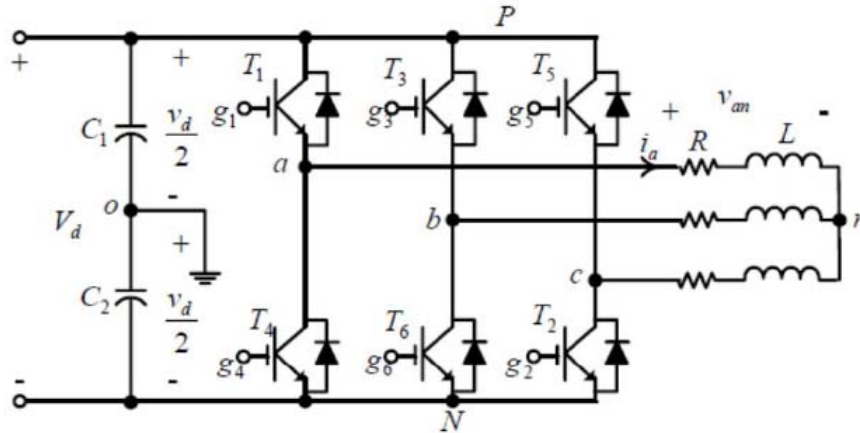
### Question 3

In the three-phase full bridge inverter shown below, the dc voltage  $V_d = 300$  V, the amplitude modulation index  $m_a = 0.8$ , the frequency modulation index  $m_f = 39$ , and the frequency of three-phase sine modulating wave is 60 Hz. The load is three-phase Y-connected RL load, the resistance is  $10 \Omega$  and the inductance is 28 mH. Answer the following questions.



- 1) Determine the rms values of the output line-to-line voltage and line current at fundamental frequency.

$$V_{LL,1} = \underline{147} \text{ V}$$

$$I_{L,1} = \underline{5.84} \text{ A}$$

Solution:

From table 8-2,

$$V_{LL,1} = 0.49V_d = 0.49 \times 300 = 147 \text{ V}$$

$$Z = \sqrt{R^2 + (\omega L)^2} = \sqrt{10^2 + (2 \times \pi \times 60 \times 28 \times 10^{-3})^2} = 14.54 \Omega$$

$$I_{L,1} = \frac{V_{LL,1}/\sqrt{3}}{Z} = \frac{147/\sqrt{3}}{14.54} = 5.84 \text{ A}$$

- 2) Calculate the output power considering only fundamental component.

$$P_{out} = \underline{1.02} \text{ kW}$$

Solution:

$$\text{Load angle } \theta = \tan^{-1} \frac{2\pi f L}{R} = \tan^{-1} \frac{2\pi \times 60 \times 28 \times 10^{-3}}{10} = 46.55^\circ$$

$$\text{PF} = \cos \theta = \cos 46.55^\circ = 0.6877$$

$$P_{out} = \sqrt{3} V_{LL,1} I_{L,1} \times \text{PF} = \sqrt{3} \times 147 \times 5.84 \times 0.6877 = 1.02 \text{ kW}$$

or

$$P_{out} = 3 I_{L,1}^2 R = 3 \times 5.84^2 \times 10 = 1.02 \text{ kW}$$